

① Phase-Locked Loop (PLL)

The PLL is a feedback control system that can synchronize the instantaneous phase of an oscillator output with that of a reference signal.

The main components of a PLL are:

- 1) Voltage-controlled Oscillator (VCO)
- 2) Phase detector or Phase comparator
- 3) Loop filter

VCO

The instantaneous frequency of VCO output is proportional to the control input voltage.


$$\boxed{\omega_i(t) = \omega_0 + K_v \cdot e_v(t)}$$

①

$\omega_i(t)$ - instantaneous frequency of the VCO output

K_v - VCO constant

$e_v(t)$ - Control voltage

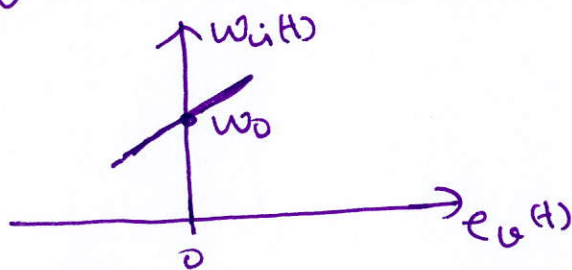


ω_0 , the frequency of the VCO output when the control voltage is zero, is called the free-running frequency of the VCO.

Instantaneous phase

$$\boxed{\int_0^t \omega_i(\tau) d\tau = \omega_0 t + K_v \int_0^t e_v(\tau) d\tau}$$


②

(2)

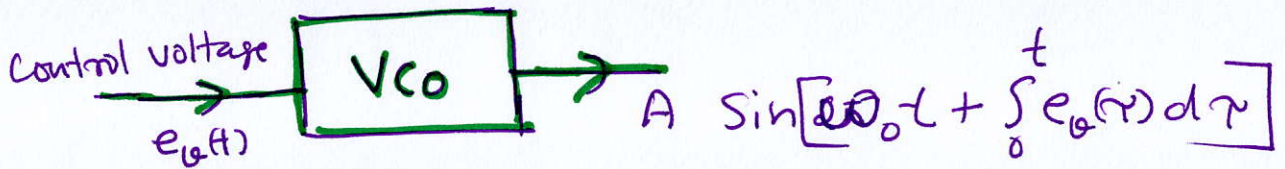


Phase Detector

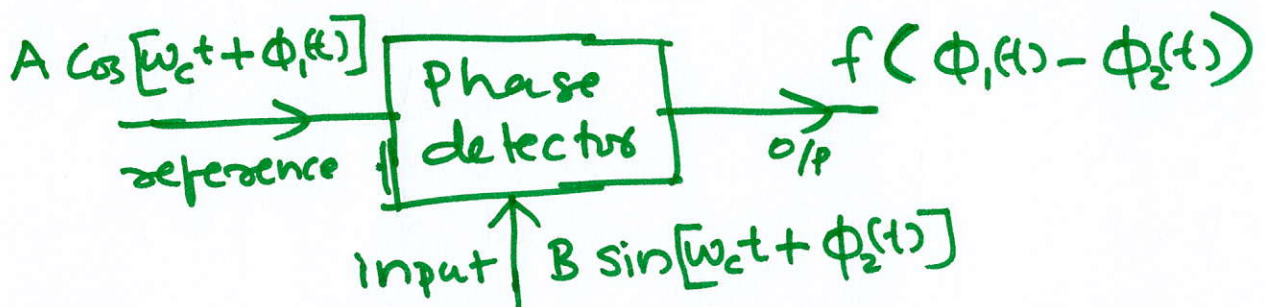The phase detector compares the instantaneous phase of the input signal with that of a reference signal and produces an output that is a function of the phase difference.



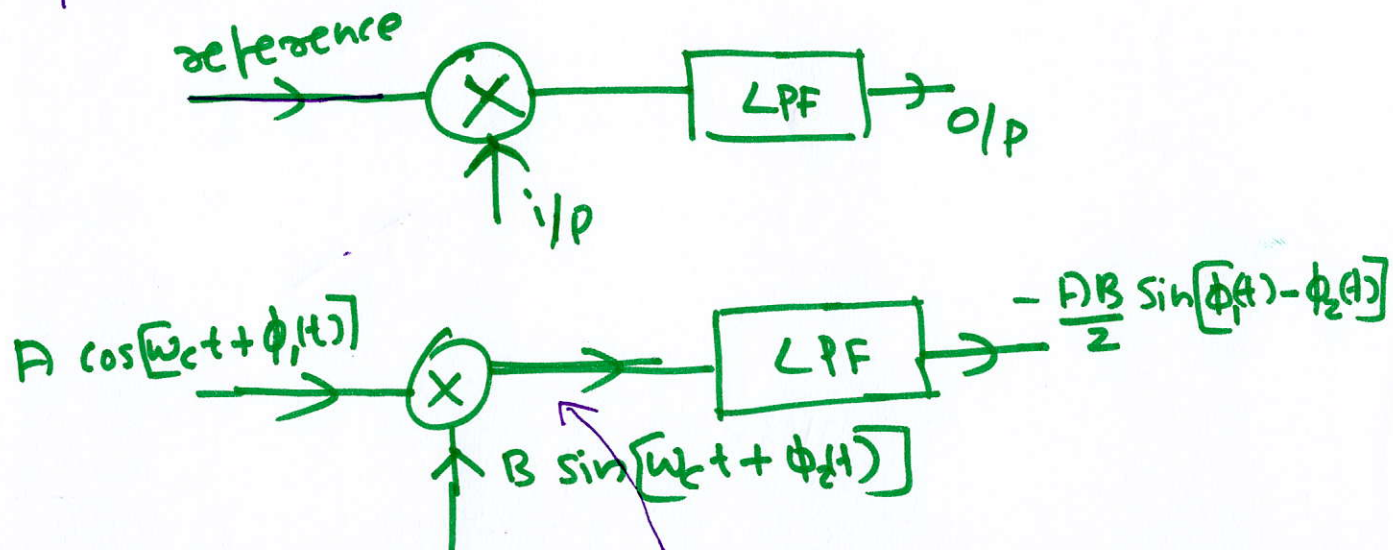We consider the following realization of phase detector.




The mixer (multiplier) output is

$$\frac{AB}{2} \sin[2\omega_c t + \phi_1(t) + \phi_2(t)] - \frac{AB}{2} \sin[\phi_1(t) - \phi_2(t)]$$

↑
removed by the LPF

The loop filter is a low pass filter whose role is explained later

Block diagram of PLL

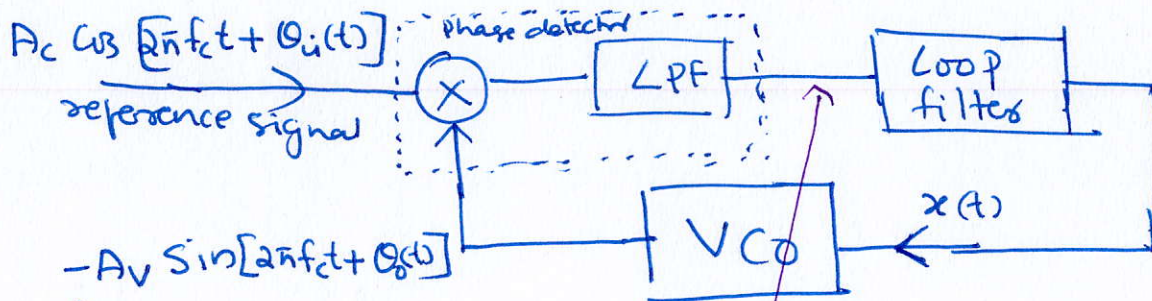

↑
-ve sign is to make the product modulator o/p +ve.

The phase detector o/p is given by,


$$\frac{A_c A_v}{2} \sin[\theta_i(t) - \theta_o(t)]$$

~~The relations between $\theta_o(t)$ and $\theta_i(t)$ and $x(t)$ are~~


$\theta_o(t)$ and the VCO control i/p $x(t)$ are related by

$$\theta_o(t) = K_v \int_0^t x(\tau) d\tau$$

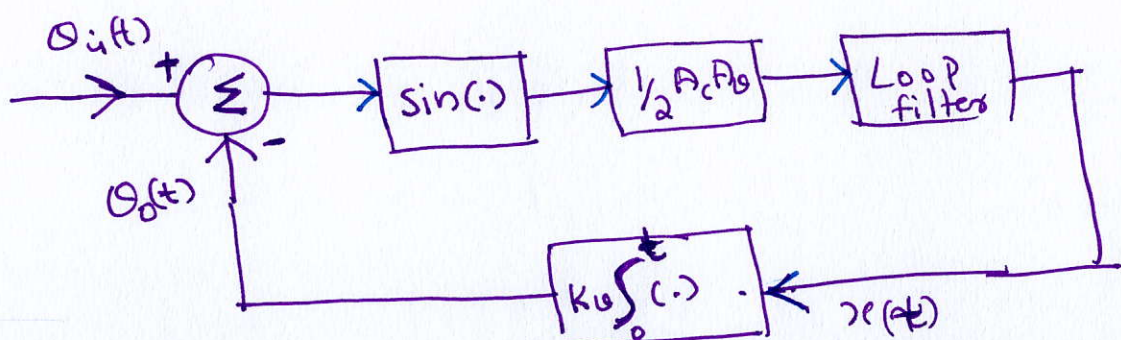Since we are interested in the relation between $\theta_i(t)$ and $\theta_o(t)$, the PLL can be modeled as



(4)

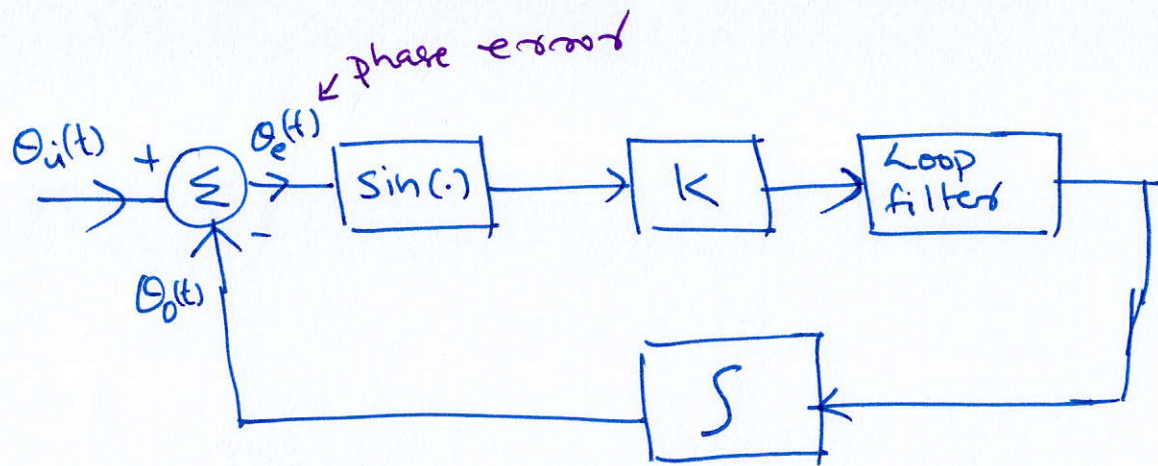

$$K = \frac{1}{2} A_c A_v K_o \text{ is the loop gain}$$


This is a negative feedback control system. The analysis of this system is difficult due to the $\sin(\cdot)$ non-linearity.

Linear approximation of PLL

When $\theta_i(t) \approx \theta_o(t)$

$$\sin[\theta_i(t) - \theta_o(t)] \approx \theta_i(t) - \theta_o(t)$$

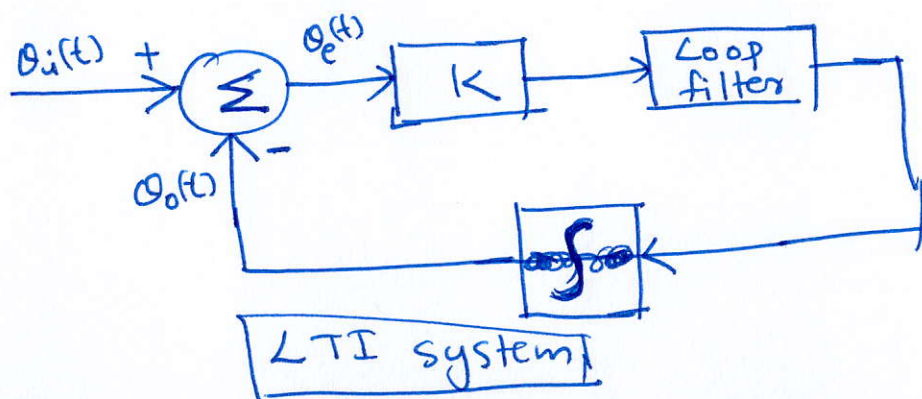This approximation results in the following linear model.




We can analyze the system in the Laplace-domain.

$$\theta_i(t) \xrightarrow{LT} \Theta_i(s) ; \theta_o(t) \xrightarrow{LT} \Theta_o(s)$$

$$\text{integrator} \rightarrow \boxed{1/s}$$

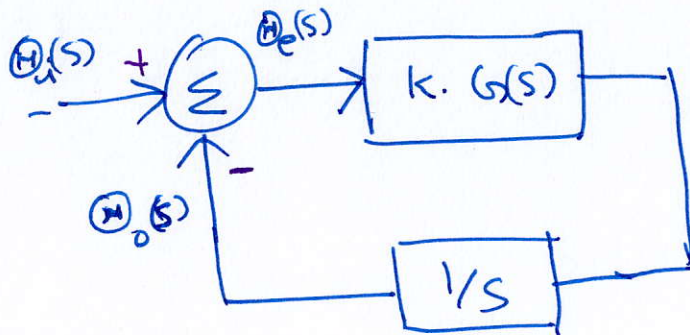(5)

Assuming that the system function of the loop filter is $G(s)$, the s-domain model of linearized PLL can be represented as



The transfer function $H(s) = \frac{M_o(s)}{M_i(s)}$

$$M_o(s) = [M_i(s) - M_o(s)] \cdot \frac{K \cdot G(s)}{s}$$

$$\therefore H(s) = \frac{K G(s)}{s + K G(s)} \quad (3)$$

The error-transfer function

$$H_e(s) = \frac{M_e(s)}{M_i(s)} = \frac{M_i(s) - M_o(s)}{M_i(s)}$$

$$\therefore H_e(s) = 1 - H(s)$$

$$= \frac{s}{s + K G(s)} \quad (4)$$

First-order PLL

For first-order PLL, $G(s) = 1$

$$\therefore H(s) = \frac{K}{s + K} \quad (5)$$

$$H_e(s) = \frac{s}{s + K} \quad (6)$$

⑥

Let us now analyze how a first-order PLL synchronize $\theta_i(t)$ and $\theta_o(t)$.

Remember,

instantaneous phase of the input reference signal
 $2\pi f_c t + \theta_i(t)$

instantaneous phase of the ~~out~~ VCO output
 $2\pi f_c t + \theta_o(t)$

instantaneous phase error

$$\begin{aligned}\theta_e(t) &= [2\pi f_c t + \theta_i(t)] - [2\pi f_c t + \theta_o(t)] \\ &= \theta_i(t) - \theta_o(t)\end{aligned}$$

First, we considered how the PLL tracks a sudden change (step change) in the phase of the reference signal.



$$\text{Let } \theta_i(t) = \Delta\theta u(t)$$

i.e., the reference signal is

$$A \cos [2\pi f_c t + \Delta\theta u(t)]$$

where $u(t)$ is the unit step function

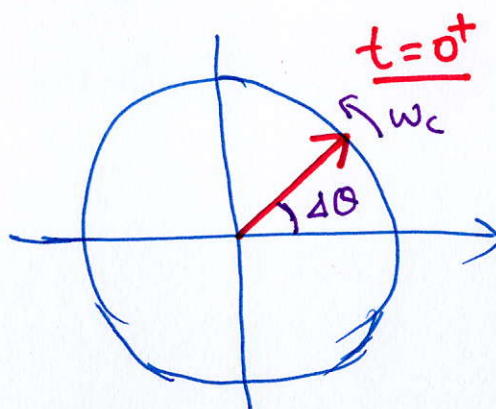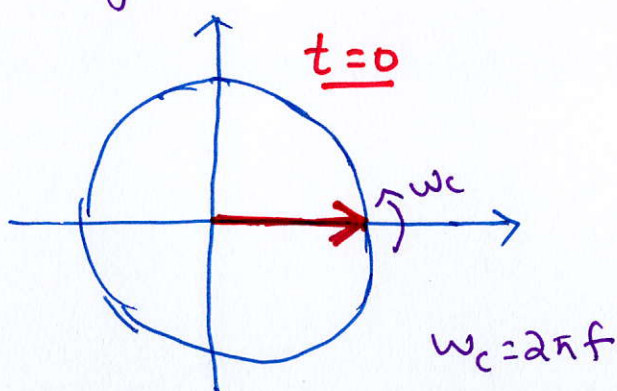The phasor corresponding to this reference signal can be represented as



7

$$\theta_i(t) = \Delta\theta u(t)$$

$$u(t) \xrightarrow{\mathcal{L}\mathcal{T}} \frac{1}{s}$$

$$\Theta_i(s) = \frac{\Delta\theta}{s}$$

$$H(s) = \frac{\Theta_o(s)}{\Theta_i(s)} = \frac{K}{s+K} \quad \leftarrow \text{from 5}$$



$$\therefore \Theta_o(s) = H(s) * \Theta_i(s) = \frac{K}{s+K} \cdot \frac{\Delta\theta}{s}$$

$$\Theta_o(s) = \Delta\theta \left[\frac{1}{s} - \frac{1}{s+K} \right]$$

$$e^{-Kt} u(t) \xrightarrow{\mathcal{L}\mathcal{T}} \frac{1}{s+K}$$

Taking the inverse $\mathcal{L}\mathcal{T}$,
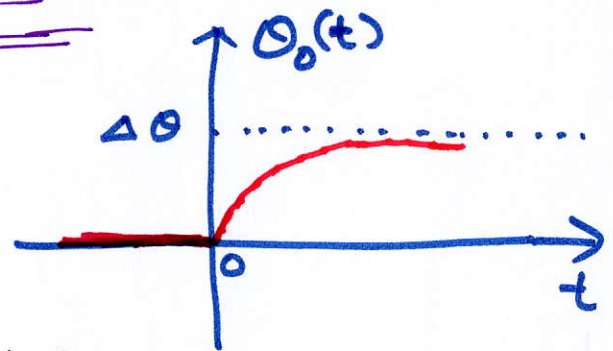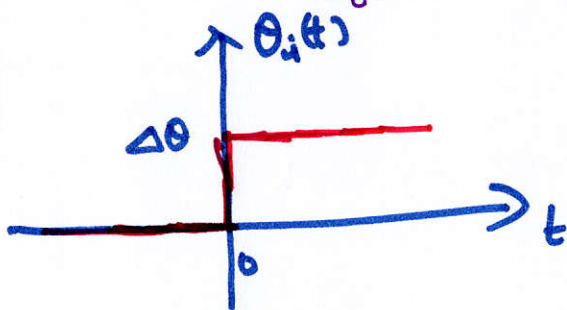
$$\theta_o(t) = \Delta\theta [1 - e^{-Kt}] u(t)$$



In the steady state

$$\lim_{t \rightarrow \infty} \theta_o(t) = \Delta\theta$$

$$\therefore \lim_{t \rightarrow \infty} \theta_e(t) = 0 \quad \boxed{\text{phase error}}$$

Thus, the first-order PLL can track a sudden change in phase, with the output phase converging to the input phase exponentially fast. The steady state phase error is zero.


Note: Increasing the loop gain K increases the rate of convergence of the output phase.

⑧

We now consider how the first-order PLL tracks a step change in the frequency of the reference signal.

Let the instantaneous frequency of the reference signal is


$$f_i(t) = f_c + \Delta f u(t)$$

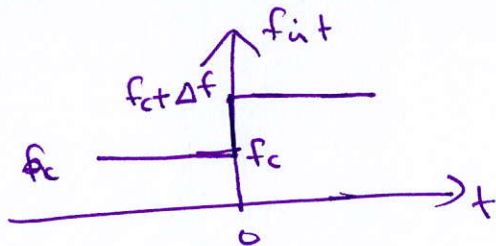

The reference signal is

$$A_c \cos[2\pi f_c t + 2\pi \Delta f t u(t)]$$
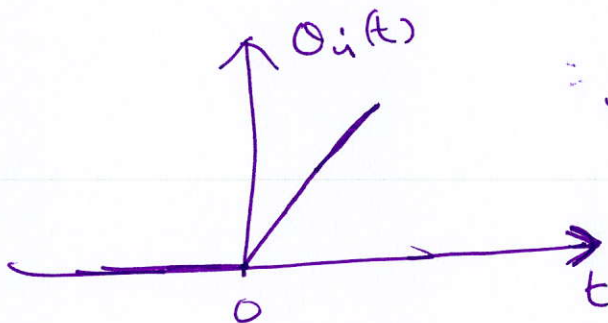
$$\therefore \theta_i(t) = 2\pi \Delta f t u(t)$$



ie. linear change in the phase.

$$\theta_i(t) = 2\pi \Delta f t u(t)$$

$$\Theta_i(s) = \frac{2\pi \Delta f}{s^2} \quad \textcircled{7}$$

$$t u(t) \xrightarrow{\mathcal{L}} \frac{1}{s^2}$$

$$\therefore \Theta_o(s) = H(s) \cdot \Theta_i(s)$$

$$\Theta_o(s) = \frac{K}{s+K} \cdot \frac{2\pi \Delta f}{s^2} \quad \textcircled{8}$$

from $\textcircled{5}$

(9)

Let us first consider how the PLL tracks the ~~ch~~ instantaneous frequency.

Instantaneous frequency of the VCO output,

$$f_o(t) = \frac{1}{2\pi} \frac{d}{dt} [2\pi f_c t + \theta_o(t)]$$

$$= f_c + \frac{1}{2\pi} \frac{d}{dt} \theta_o(t)$$

$$\theta_o(t) \xrightarrow{LT} \Theta_o(s)$$

$$\frac{d}{dt} \theta_o(t) \xrightarrow{LT} s \Theta_o(s)$$


From (8),

$$\frac{1}{2\pi} \frac{d}{dt} \theta_o(t) \xrightarrow{LT} \frac{K}{s+k} \frac{\Delta f}{s} = \Delta f \left(\frac{1}{s} - \frac{1}{s+k} \right)$$


taking the inverse LT, we get

$$\frac{1}{2\pi} \frac{d}{dt} \theta_o(t) = \Delta f (1 - e^{-kt}) u(t)$$
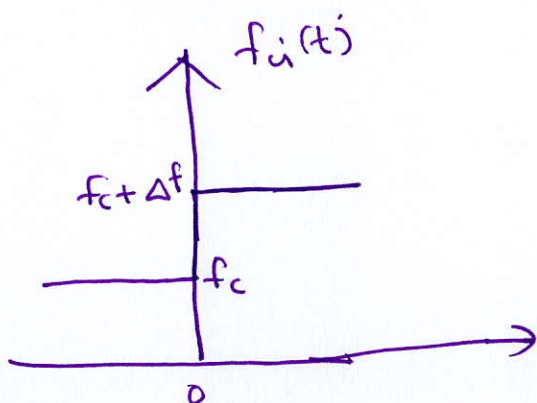
$$\therefore f_o(t) = f_c + \Delta f (1 - e^{-kt}) u(t)$$



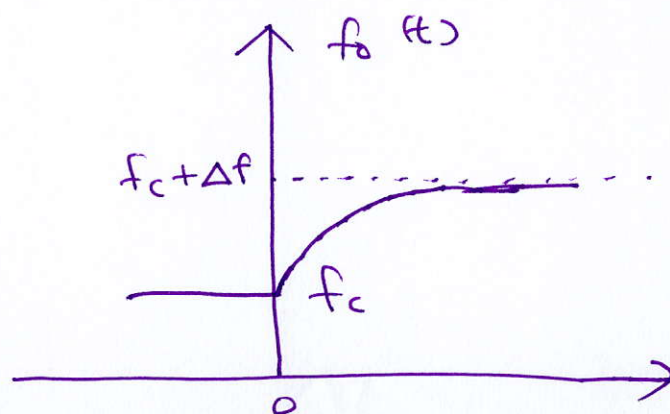instantaneous freq. of the reference signal



instantaneous freq. of the VCO output

\therefore The first order PLL tracks step change in frequency, ^{converging} exponentially fast.

~~It is rate~~

We now analyze ~~the~~ how the PLL tracks instantaneous phase.

$$H_e(s) = \frac{(H)_e(s)}{(H)_i(s)} = \frac{\cancel{b}s}{s+k} \quad \leftarrow \text{from (6)}$$

$\leftarrow \text{from (8)}$

$$(H)_e(s) = \frac{\cancel{b}s}{s+k} (H)_i(s) = \frac{\cancel{b}s}{s+k} \cdot \frac{2\pi\Delta f}{s^2}$$

By using the final value theorem

$$\lim_{t \rightarrow \infty} \theta_e(t) = \lim_{s \rightarrow 0} s (H)_e(s) \quad \leftarrow$$

$$= \frac{2\pi\Delta f}{K}$$



i.e. there is a steady state phase error.

We can summarize,

If there is a step change in frequency of the reference signal, the first-order PLL tracks the change in frequency, but there is a steady state phase error.

In terms of phase

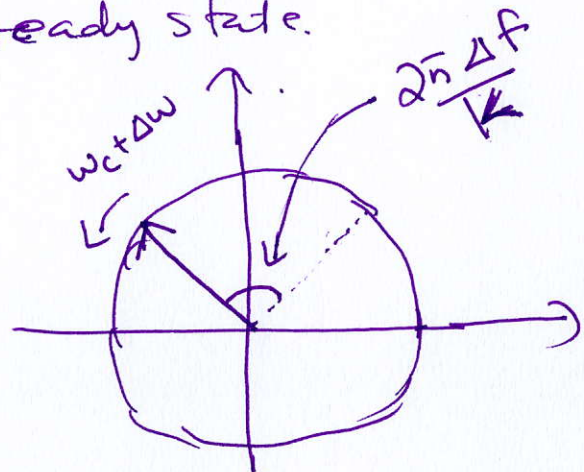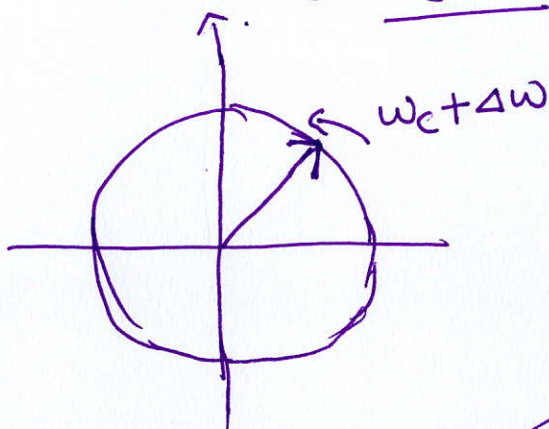$t = t_0 \gg 0 \leftarrow \text{steady state.}$



$$\boxed{\begin{aligned} \omega_c &= 2\pi f_c \\ \Delta\omega &= 2\pi\Delta f \end{aligned}}$$

This problem, i.e. steady state phase error, can be ~~be~~ solved if we use a second order PLL.

The transfer function $G(s)$ of ~~the~~ a second order PLL is given by

$$\underline{\underline{G(s) = \frac{s+a}{s}}}$$

Exercise: Show that the steady-state phase error ($\lim_{t \rightarrow \infty} \phi_e(t)$) is ~~zero~~ ~~if we~~ ~~use a~~ ~~s~~ for second order PLL