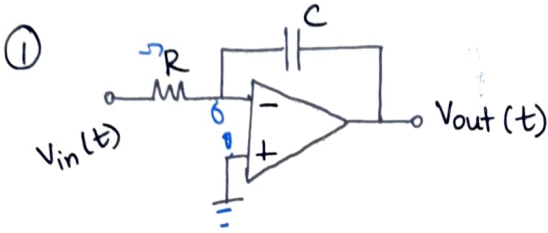


# Tutorial - 3

19 August 2024 12:18




Assume an ideal opamp.

Derive the expression for  $V_{out}(t)$  in terms of  $V_{in}(t)$ ,  $R$  and  $C$ .

If  $V_{in}(t) = A \cos(2\pi f t)$ , Calculate  $V_{out}$ .

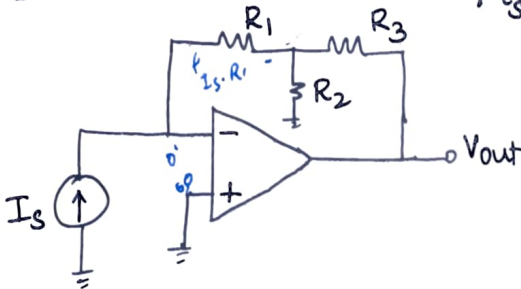
② Determine the ratio  $V_o/i_s$  in the opamp circuit below.



Evaluate the "transresistance" for  $R_1 = 20 \text{ k}\Omega$ ,  $R_2 = 25 \text{ k}\Omega$  and  $R_3 = 40 \text{ k}\Omega$

③ Realize the following expression using the minimum number of opamps and resistors.  $V_1$  &  $V_2$  are input voltages.

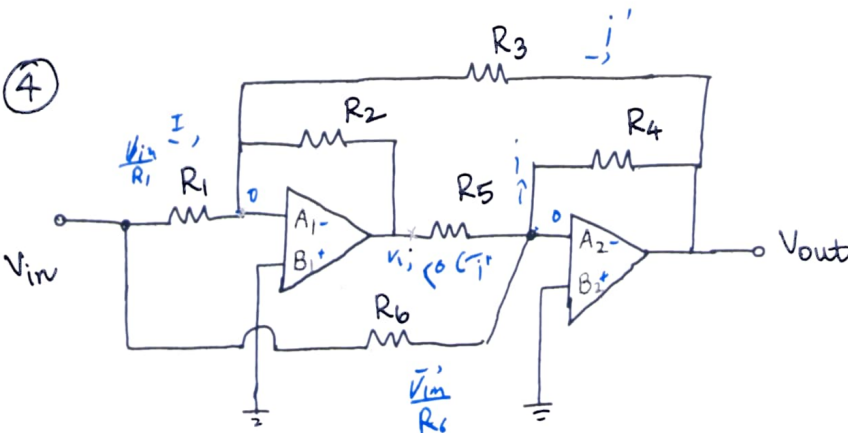
$$V_o = \frac{(R_3 + R_4)}{R_3(R_1 + R_2)} (R_2 V_1 + R_1 V_2)$$



(a) Determine the signs of the opamp (where  $A_1$  or  $B_1$  is positive or negative) for negative feedback. Note that when multiple loops are involved, the procedure is to ensure every loop is in negative feedback.

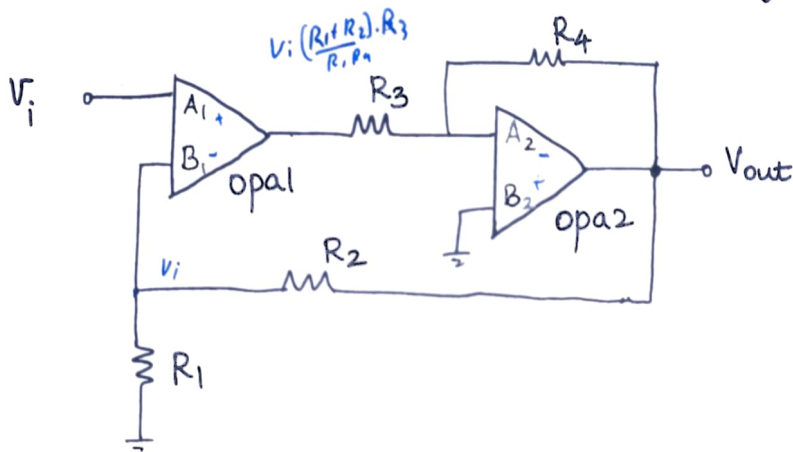
(b) Calculate  $V_{out}/V_{in}$ .

⑤ Determine the signs of the opamp for negative f/b.



Calculate  $V_{out}/V_i$

⑥

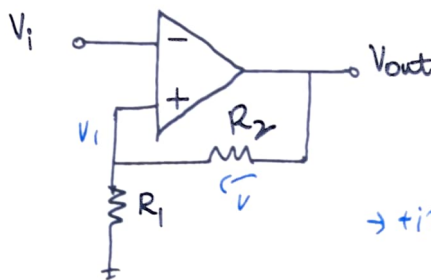

$$\begin{aligned}
 V_{out} &= \frac{V_i \cdot R_2}{R_1} + V_i \\
 &= V_i \left( \frac{R_2 + R_1}{R_1} \right) \\
 &= 2 \cdot V_i
 \end{aligned}$$

→ +ive feedback

Calculate  $V_{out}$ , when  $R_1 = R_2 = 1k\Omega$   
and  $V_i = 1V$