

**INDIAN INSTITUTE OF TECHNOLOGY ROORKEE  
MID/END TERM EXAMINATION**

Name of the student ..... Ecc-205 Answer Key. Programme .....



Course Code ..... Course Name .....

Date of Exam ..... Enrollment No ..... Signature of Invigilator .....

Set-B

- ① Number of dependent variables = Order of the circuit.  
 $C_4$  &  $L_3$  does not come in the picture for calculating order.  
 $\Rightarrow$  Order = 6

②

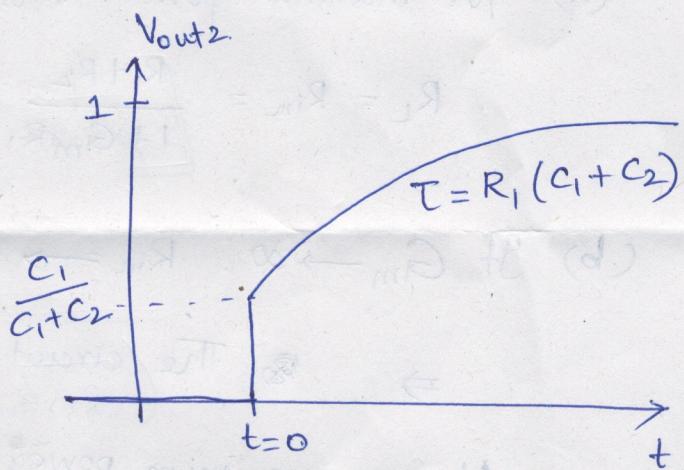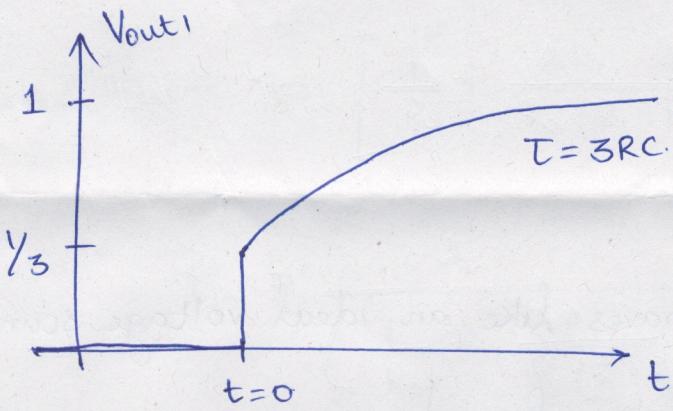

$$\frac{C_1}{C_1+C_2} = \frac{1}{3} \Rightarrow 3C_1 - C_1 = C_2$$

$$C_1 = C_2/2.$$

$$R_1(C_1 + C_2) = 3RC$$

$$R_1 \cdot 1.5C_2 = 3RC$$

$$C_2 = C$$


$$\Rightarrow R_1 = 2R$$


$$R_1 = 2R$$

$$C_1 = C/2$$

$$C_2 = C$$

- ④ B is negative, A is positive.

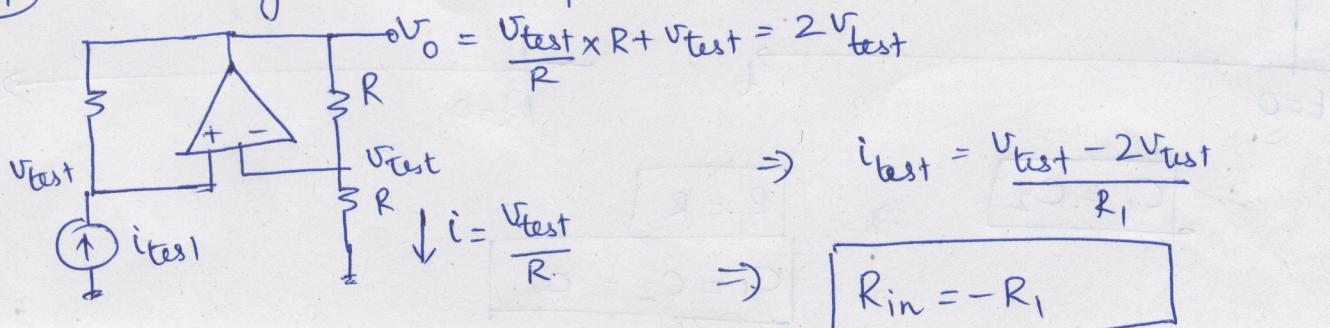

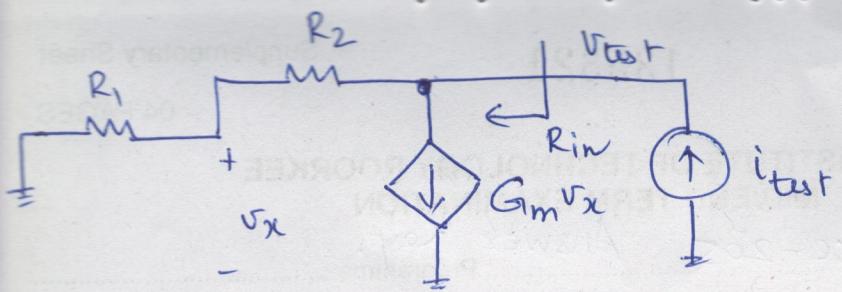

$$v_{test} = G_m v_x + \frac{v_{test}}{R_1 + R_2} = G_m \cdot \frac{v_{test} R_1}{R_1 + R_2} + \frac{v_{test}}{R_1 + R_2}$$

$$R_{in} = \frac{v_{test}}{i_{test}} = \frac{1 \times (R_1 + R_2)}{(1 + G_m R_1)}$$

for maximum power transfer.



$$R_L = R_{in} = \frac{R_1 + R_2}{1 + G_m R_1}$$

if  $G_m \rightarrow \infty$ ,  $R_{in} \rightarrow 0$

$\Rightarrow$  The circuit behaves like an ideal voltage source.

Always maximum power is transferred.

Order = 7

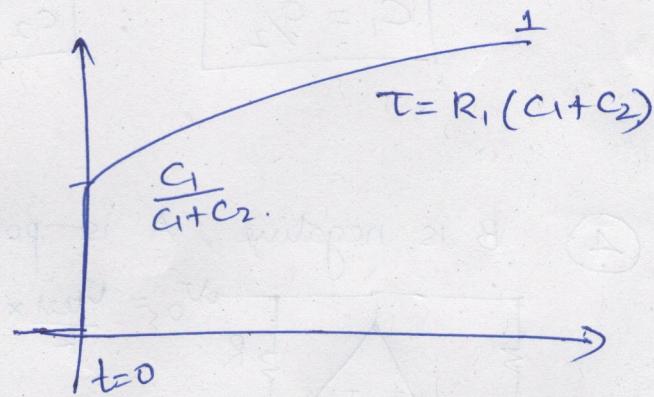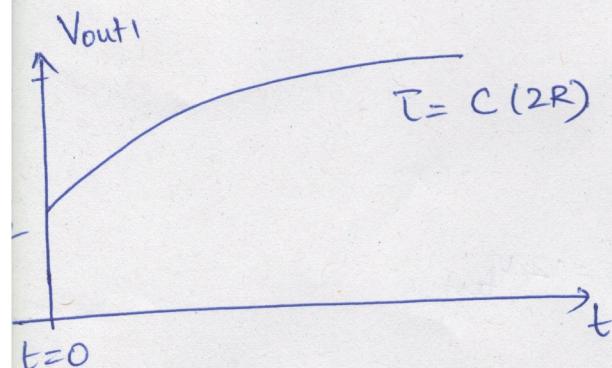


$$\therefore C_1 = C_2$$

$$\Rightarrow R_1 = R$$

④ A is negative, B is positive.

$$\therefore R_{in} = -R_1 \quad (\text{same as before}).$$

⑤

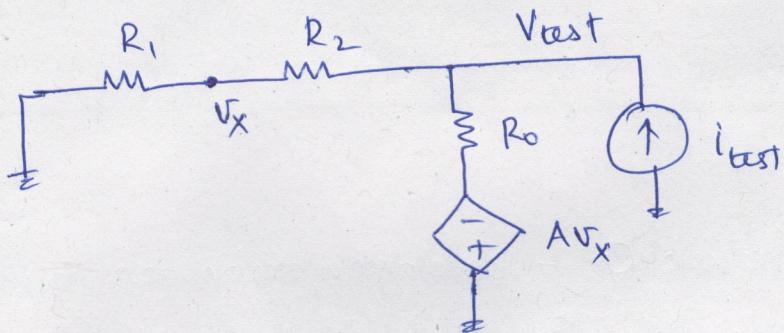

$$\therefore V_x = V_{\text{test}} \cdot \frac{R_1}{R_1 + R_2} \quad i_{\text{test}} = \frac{V_{\text{test}} + A \frac{R_1}{R_1 + R_2} V_x}{R_o} + \frac{V_{\text{test}}}{R_1 + R_2}$$

$$i_{\text{test}} = V_{\text{test}} \left[ \frac{1}{R_o} + \frac{AR_1}{R_o(R_1 + R_2)} + \frac{1}{R_1 + R_2} \right]$$

$$R_{in} = \frac{1}{\left( \frac{1}{R_o} + \frac{AR_1}{R_o(R_1 + R_2)} + \frac{1}{R_1 + R_2} \right)}$$

(a)  $R_o = R_{in}$

(b)  $A \rightarrow \infty, R_{in} \rightarrow 0$

Always max power is transferred!

# IIT Roorkee: Mid Term Exam, July - Nov 2024

## ECC - 205 Network Theory (Set-B)

Time : 1.5 hours

Maximum marks : 50

### QUESTION - 1 (10 MARKS)

As discussed in class, the order of the circuit is the order of the differential equation relating the output and input of the circuit. I had also asked you (in class) to think about the relation between order and the various components of a circuit. This question deals with that thought. Fig. 1 shows a high order circuit with multiple resistors (R), capacitors (C) and inductors (L). Find the order of the circuit.

- ① Observation that capacitor voltages & inductor currents are unknowns  $\rightarrow 3$  marks
- ②  $C_4$  &  $L_3$  do not form part of unknowns  $\rightarrow 3$  marks
- ③ Order  $\Rightarrow 6$   $\rightarrow 4$  marks

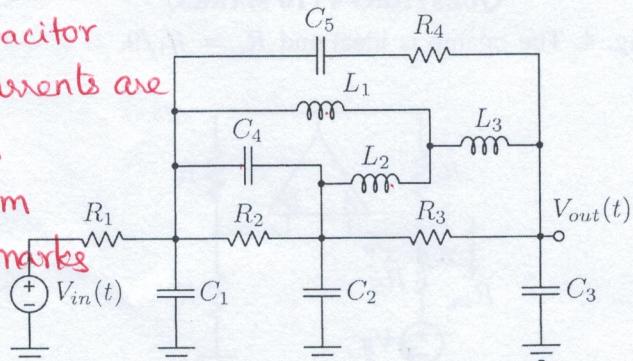


Fig. 1. Figure for question - 1

### QUESTION - 2 (10 MARKS)

Consider the circuits shown in Fig. 2(a) and Fig. 2(b). The input is a unit step signal for both the circuits. Assume zero initial conditions in the capacitors.

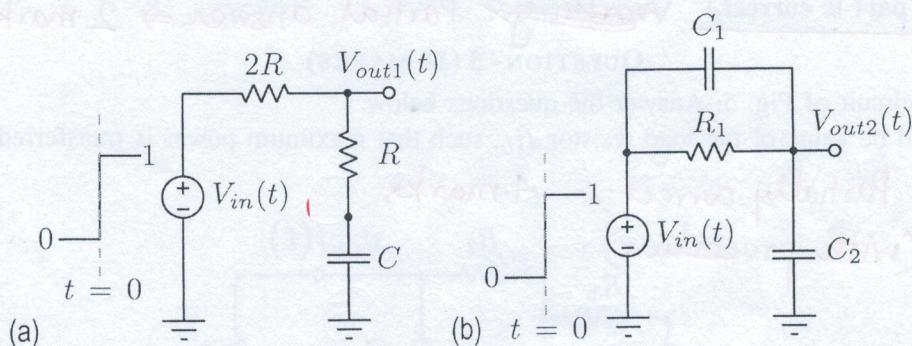


Fig. 2. Figure for question - 2

- Sketch the output voltage,  $V_{out1}(t)$  as a function of time. What is the time constant of the circuit? (5 marks) **correct o/p voltage  $\rightarrow 3$  marks, correct time constant  $\rightarrow 2$  marks**
- Fig. 2(b) is another circuit, whose output is  $V_{out2}(t)$ . Can  $V_{out2}$  be made to have the same response (with time) as  $V_{out1}$ ? If yes, then what are the values of  $R_1$ ,  $C_1$  and  $C_2$  to achieve the same? If not, then justify your claim. (5 marks)

\* Observing that (b) can give the same o/p as  $V_{out1}$  & its shape correct :- 2 marks

\* Correct  $R_1 \rightarrow 1$  mark,  $C_1 \rightarrow 1$  mark,  $C_2 \rightarrow 1$  mark.

(Laplace domain)

Correct Tellegen equation  $\sum V_k(s) \hat{I}(s) = 0 \Rightarrow \sum \hat{V}_k(s) \hat{I}_k(s) = 0 \Rightarrow 5 \text{ marks}$

### QUESTION - 3 (10 MARKS)

The network  $N$  contains only resistors, capacitors and inductors. Assume the initial conditions are zero for all the components in the network.

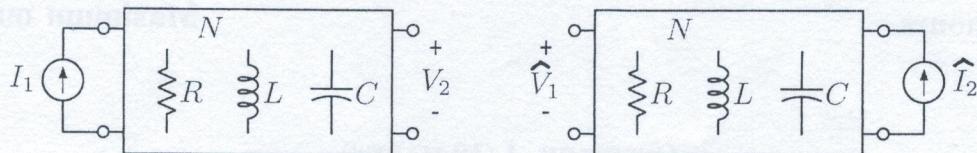


Fig. 3. Figure for question - 3

Can you prove that the network is reciprocal (i.e)  $V_2/I_1 = \hat{V}_1/\hat{I}_2$ ? [Hint : Follow the steps of the proof of reciprocity theorem in the Laplace domain.]

### QUESTION - 4 (10 MARKS)

Consider the circuit of Fig. 4. The opamp is ideal and  $R_s = R_1/9$ .

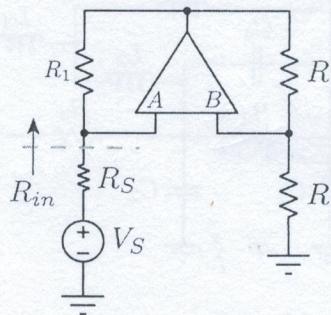


Fig. 4. Figure for question - 4

- Determine the signs of the opamp for negative feedback. (5 marks) [Hint: Calculate the loop gain by breaking the loop at the output of the opamp.] **B is -ve & A is +ve  $\Rightarrow 5$  marks.**
- Determine  $R_{in}$ , the resistance seen by the current source  $I_{in}$ . (5 marks. Credit will be given only if the first part is correct.) **~~Working & Partial answer  $\Rightarrow 2$  marks, full answer  $\Rightarrow 5$  marks.~~**

### QUESTION - 5 (10 MARKS)

Consider the circuit of Fig. 5. Answer the questions below.

- What should be value of the load resistor  $R_L$ , such that maximum power is transferred to the load? (7 marks)

**Partially correct :- 4 marks  
(with procedure)**

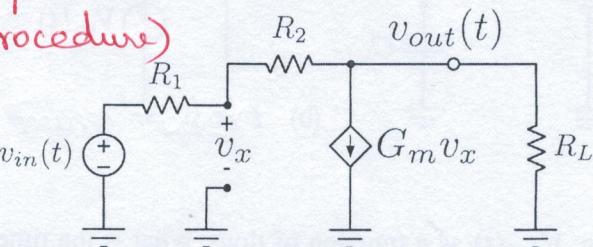


Fig. 5. Figure for question - 5

- If  $G_m$  tends to infinity, what is the optimum load  $R_L$ , such that maximum power is transferred? Explain your result intuitively. (3 marks)

**Circuit approaches an ideal voltage source & maximum power is always transferred  $\rightarrow 3$  marks.**

# IIT Roorkee: Mid Term Exam, July - Nov 2024

## ECC - 205 Network Theory (Set-A)

Time : 1.5 hours

Maximum marks : 50

### QUESTION - 1 (10 MARKS)

As discussed in class, the order of the circuit is the order of the differential equation relating the output and input of the circuit. I had also asked you (in class) to think about the relation between order and the various components of a circuit. This question deals with that thought. Fig. 1 shows a high order circuit with multiple resistors (R), capacitors (C) and inductors (L). Find the order of the circuit.

Observation that capacitor voltage

& inductor currents are unknowns → 3 marks

C<sub>4</sub> & L<sub>4</sub> do not form part of unknowns → 3 marks

Order = 7 → 4 marks

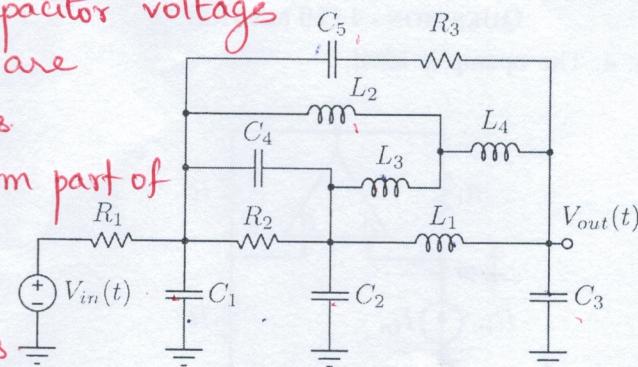


Fig. 1. Figure for question - 1

### QUESTION - 2 (10 MARKS)

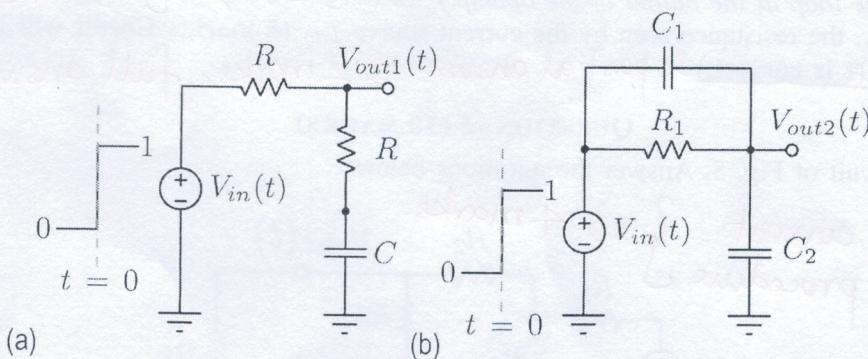


Fig. 2. Figure for question - 2

Consider the circuits shown in Fig. 2(a) and Fig. 2(b). The input is a unit step signal for both the circuits. Assume zero initial conditions in the capacitors.

- Sketch the output voltage,  $V_{out1}(t)$  as a function of time. What is the time constant of the circuit? (5 marks)
- Fig. 2(b) is another circuit, whose output is  $V_{out2}(t)$ . Can  $V_{out2}$  be made to have the same response (with time) as  $V_{out1}$ ? If yes, then what are the values of  $R_1$ ,  $C_1$  and  $C_2$  to achieve the same? If not, then justify your claim. (5 marks)

Correct o/p voltage → 3 marks, correct time constant → 2 marks

\* Observing that (b) can give the same o/p as  $V_{out1}$  & its shape is correct :- 2 marks

\* Correct R<sub>1</sub> → 1 mark, C<sub>1</sub> → 1 mark, C<sub>2</sub> → 1 mark.

(Laplace domain)

Correct Tellegen equation  $\sum V_k(s) \hat{I}_k(s) = \sum \hat{V}_k(s) I_k(s) = 0$

### QUESTION - 3 (10 MARKS)

Consider the network  $N$  shown in Fig. 3. It contains only resistors, capacitors and inductors. Assume the initial conditions are zero for all the components in the network. Can you show that the network is reciprocal (i.e.)  $V_2/I_1 = \hat{V}_1/\hat{I}_2$ ? [Hint: Follow the steps of the proof of reciprocity theorem in the Laplace domain.]

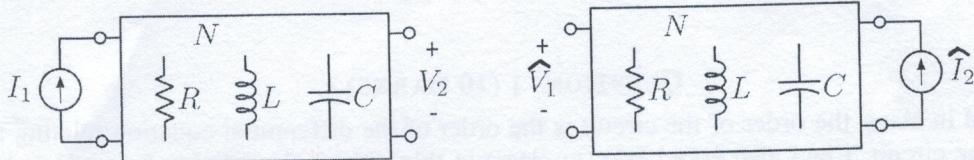


Fig. 3. Figure for question - 3

### QUESTION - 4 (10 MARKS)

Consider the circuit of Fig. 4. The opamp is ideal.

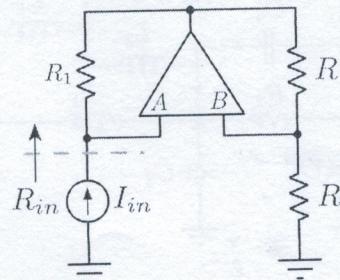


Fig. 4. Figure for question - 4

- Determine the signs of the opamp for negative feedback. (5 marks) [Hint: Calculate the loop gain by breaking the loop at the output of the opamp.]  $A$  is -ve &  $B$  is +ve  $\Rightarrow$  5 marks
- Determine  $R_{in}$ , the resistance seen by the current source  $I_{in}$ . (5 marks. Credit will be given only if the first part is correct) & partial answer  $\Rightarrow$  2 marks, full answer  $\Rightarrow$  5 marks.

### QUESTION - 5 (10 MARKS)

Consider the circuit of Fig. 5. Answer the questions below.

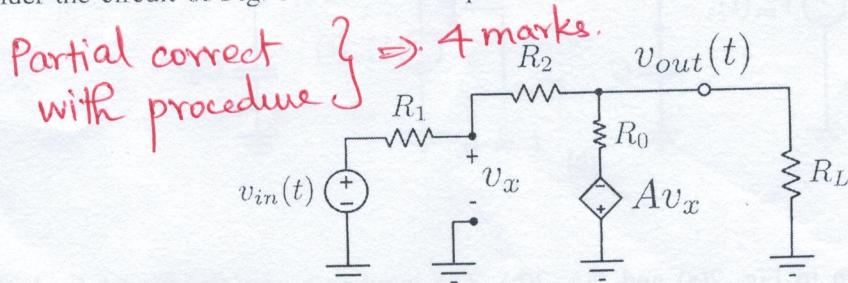


Fig. 5. Figure for question - 5

- What should be value of the load resistor  $R_L$ , such that maximum power is transferred to the load? (7 marks)
- If the gain of the VCVS,  $A$ , tends to infinity, what is the optimum load  $R_L$ , such that maximum power is transferred? Explain your result intuitively. (3 marks)

Circuit approaches an ideal voltage source & maximum power is always transferred  $\rightarrow$  3 marks.