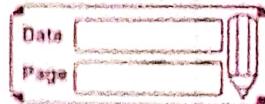



$$\nabla \cdot D = S$$

$$D = \epsilon F + P$$



FCC - 203

Transmission Lines

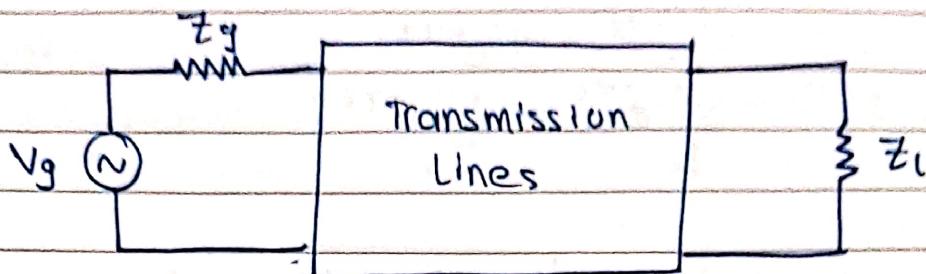

Transmission lines are two-port network connecting generator to load.

Effects of transmission lines like phase shift
\$ reflections become significant when $L \geq 10^{-3} \lambda$

Transmission Lines \rightarrow Transverse Electromagnetic (TEM)



E \$ H are perpendicular

Higher Order Lines to the wave propagation dirⁿ

A significant component (have 2 parallel conductors) in dirⁿ of wave propagation Ex. Coaxial line, Two-wire ex. Optical Fibre, Line, Parallel-Plate line, Microstrip line.

Lumped Element Circuit Model

We break the transmission line in components with:

R : series Resistance (Ω/m)

L : series Inductance (H/m)

G : shunt conductance (S/m)

C : Shunt capacitance (F/m)

By applying KCL & KVL to the lumped element model, we get Telegrapher's equations.

$$V(z) = V_o^+ e^{-\gamma z} + V_o^- e^{+\gamma z}$$

$$I(z) = \frac{V_o^+ e^{-\gamma z}}{Z_0} - \frac{V_o^- e^{+\gamma z}}{Z_0}$$

$$\gamma = \alpha + j\beta = \sqrt{(R+jWL)(G+jWC)}$$

$$Z_0 = \sqrt{\frac{R+jWL}{G+jWC}}$$

$$v(z,t) = \operatorname{Re}\{v(z)e^{j\omega t}\}$$

Transmission line effects

In normal wires, we assume that the voltage given on one end immediately reflects on the other end with exact same amplitude, but when length of wires is longer than "1/4th of wavelength" transmission line effects play a role:

→ Signal delay / Phase shift

→ Reflections and transmission with Stand SW



→ Attenuation (losses) → reflection delay & SW

→ Dispersion (different components travel at different speeds)

Signal Delay / Phase Shift


when a wave travels, if its wavelength is large compared to the length of line, there is negligible phase shifting between the 2 ends of the line.

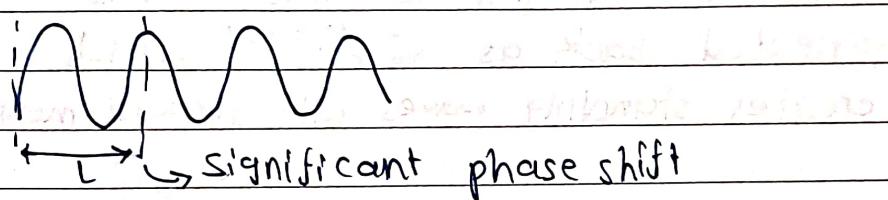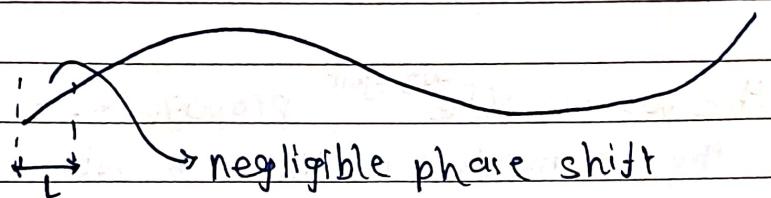But when the wavelength is comparable to the length of wire, there is a significant phase difference b/w the 2 ends.



Attenuation

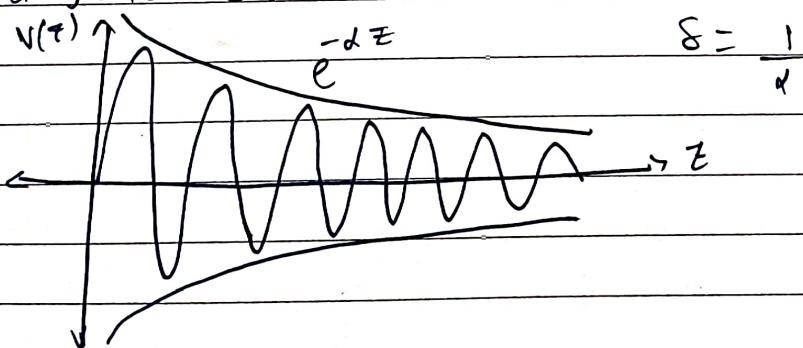The amplitude of the wave decreases as the wave propagates through transmission lines due to losses, amplitude decreases by a factor $e^{-\alpha z}$.





Dispersion

The propagation constant $M = \sqrt{(R+j\omega L)(G+j\omega C)}$ depends on the frequency ω of the propagating wave, a digital square pulse consists of various frequencies combined so different propagation constants are offered for different frequencies, so the signal gets distorted as it travels.

Reflections

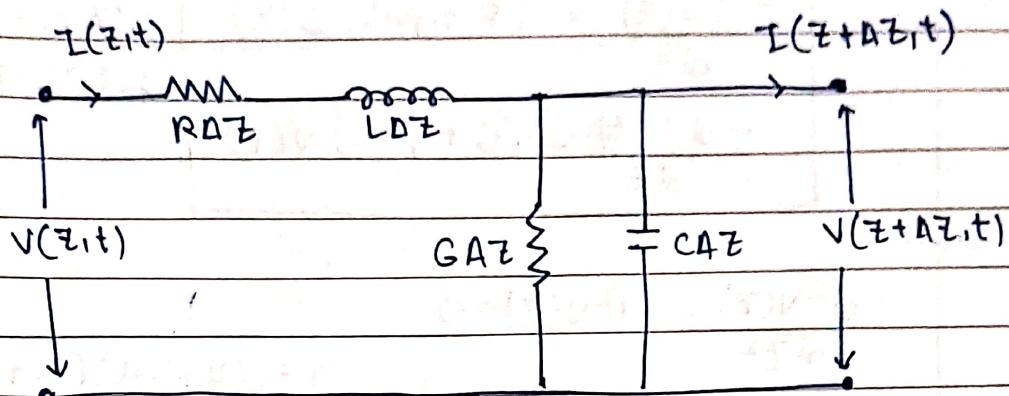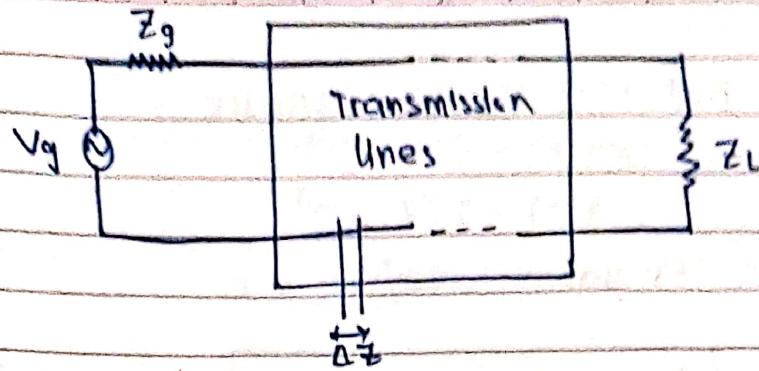When the wave $V_0 e^{j\gamma z + j\omega t}$ propagates through the transmission lines & hits the load, a part of the wave is reflected back as $V_0 e^{-j\gamma z + j\omega t}$ which creates standing waves with forward moving wave



$$V(z + \Delta z, t) = V(z, t) - I(z, t) R \Delta z - L \Delta z \frac{\partial I(z, t)}{\partial t}$$

$$\Rightarrow V(z + \Delta z, t) - V(z, t) = -I(z, t) R - L \frac{\partial I(z, t)}{\partial t} \Delta z$$

$$\Rightarrow \boxed{\frac{\partial V(z, t)}{\partial z} = -I(z, t) R - L \frac{\partial I(z, t)}{\partial t}} \quad \text{--- (1)}$$

$$I(z + \Delta z, t) = I(z, t) - G \Delta z V(z + \Delta z, t) - C \Delta z \frac{\partial V(z + \Delta z, t)}{\partial t}$$

$$\Rightarrow I(z + \Delta z, t) - I(z, t) = -G V(z + \Delta z, t) - C \frac{\partial V(z + \Delta z, t)}{\partial t} \Delta z$$

$$\Rightarrow \boxed{\frac{\partial I(z, t)}{\partial z} = -G V(z, t) - C \frac{\partial V(z, t)}{\partial t}} \quad \text{--- (2)}$$

We know that V & I are periodic in time, so $V(z, t) = V(z)e^{j\omega t}$
 $I(z, t) = I(z)e^{j\omega t}$

putting in telegrapher's eqn:

$$\begin{aligned} -\frac{dV(z)}{dz} &= (R + j\omega L) I(z) \\ -\frac{dI(z)}{dz} &= (G + j\omega C) V(z) \end{aligned}$$

$$V(z, t) = \text{Re}\{V(z)e^{j\omega t}\}$$

$$I(z, t) = \text{Re}\{I(z)e^{j\omega t}\}$$

$$\frac{d^2V(z)}{dz^2} - \gamma^2 V(z) = 0$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\frac{d^2I(z)}{dz^2} - \gamma^2 I(z) = 0$$

$$= \alpha + j\beta$$

$$Z_0 = \frac{R + j\omega L}{G + j\omega C}$$

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$$

$$I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}$$

$$= \frac{V_0^+ e^{-\gamma z}}{Z_0} - \frac{V_0^- e^{\gamma z}}{Z_0}$$

For a lossless transmission line: $R = 0, G = 0$

$$\alpha = 0, \beta = \omega \sqrt{LC}$$

$$V_p = \frac{\omega}{\beta}$$

Phase velocity

$$Z_0 = \sqrt{\frac{L}{C}}$$

In EM wave propagating in air: $R = 0$


$$G = \sigma$$

$$L = \mu$$

$$C = \epsilon$$

If V_p is independent of ω , then the line is non-dispersive.

Reflection Coefficient

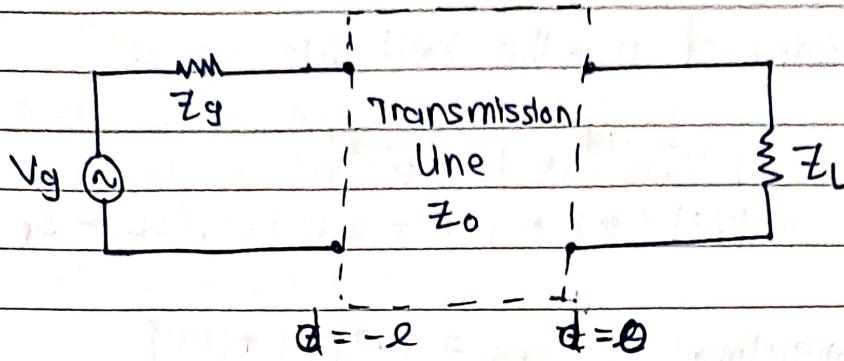

$$V(z) = V_0^+ e^{j\frac{2\pi}{\lambda} z} + V_0^- e^{-j\frac{2\pi}{\lambda} z}$$

$$I(z) = \frac{V_0^+ e^{j\frac{2\pi}{\lambda} z}}{Z_0} - \frac{V_0^- e^{-j\frac{2\pi}{\lambda} z}}{Z_0}$$

$$\text{at } \theta = 0 : V_L = V_0^+ + V_0^-$$

$$I_L = I_0^+ - I_0^- = \frac{V_0^+ - V_0^-}{Z_0}$$

$$Z_L = \frac{V_L}{I_L} = \left(\frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \right) Z_0$$

$$\boxed{\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L/Z_0 - 1}{Z_L/Z_0 + 1} = \frac{Z_L - 1}{Z_L + 1}}$$

Normalized load impedance

$$Z_L = \frac{Z_L}{Z_0}$$

As the reflection coefficient increases, the reflected wave forms a standing wave along with the incident, this results in oscillation of energy in the transmission lines rather than transfer of energy.

$$Z_L = Z_0 \quad \Gamma = 0$$

$$Z_L = 0 \quad \Gamma = -1$$

$$Z_L = \infty \quad \Gamma = 1$$

Voltage Standing Wave Ratio (SWR):

Considering ϕ from the load side, we get

$$|V(d)| = |V_0^+ e^{j\phi} + \Gamma V_0^+ e^{-j\phi}| \\ = |V_0^+| (1 + |\Gamma|^2 + 2|\Gamma| \cos(2\beta d - \Theta_r))$$

For maxima: $|V|_{\max} = |V_0^+| (1 + |\Gamma|)$

$$d_{\max} = \frac{\Theta_r \lambda}{4\pi} + \frac{n\lambda}{2}$$


$$\Gamma = |\Gamma| e^{j\Theta_r}$$

For minima: $|V|_{\min} = |V_0^+| (1 - |\Gamma|)$

$$d_{\min} = d_{\max} \pm \lambda/4$$

$S = \frac{ V _{\max}}{ V _{\min}}$	$\Gamma : 0 \rightarrow 1$
$\frac{ V _{\max}}{ V _{\min}}$	$S : 1 \rightarrow \infty$

Note: wave is moving in $+d$ direction.

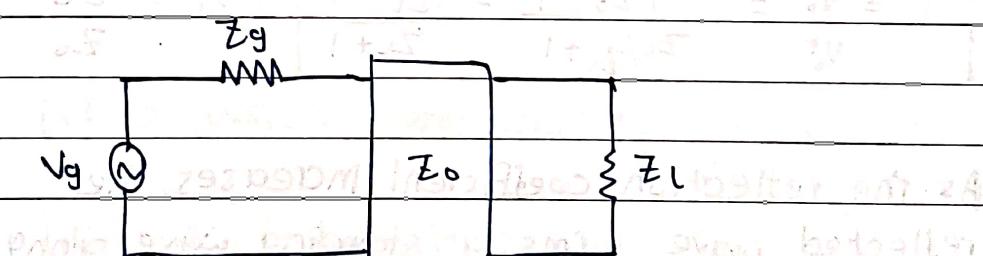

$$\theta = 7.65^\circ + j5^\circ$$

$$1 + \Gamma = 1 + 0.2633 - j0.965$$

$$1 + \Gamma = 1 + 0.2633 - j0.965$$

$$Z(d) = Z_0 \left[\frac{1 + \gamma e^{-j2Bd}}{1 - \gamma e^{-j2Bd}} \right]$$

Here d is the distance from the load terminal on the transmission line.

$$Z(0) = Z_0 \left(\frac{1 + \gamma}{1 - \gamma} \right) = Z_L$$

$$Z_{in} = Z(L) = Z_0 \left(\frac{e^{jBL} + \gamma e^{-jBL}}{e^{jBL} - \gamma e^{-jBL}} \right)$$

putting $\gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$,

$$Z_{in} = Z_0$$

$$\left(\frac{Z_L + jZ_0 \tan BL}{Z_0 + jZ_L \tan BL} \right)$$

$$Z_{in} = Z_0 \left(\frac{Z_L + j \tan BL}{1 + j Z_L \tan BL} \right)$$

Complete Transmission Line Sol'n

$$V(d) = V_0^+ e^{jd} + V_0^- e^{-jd} \quad V_0^- = \gamma V_0^+$$

$$= V_0^+ (e^{jd} + \gamma e^{-jd})$$

$$V(L) = V_{in} = V_0^+ (e^{jL} + \gamma e^{-jL})$$

$$V_{in} = \frac{V_0 Z_{in}}{Z_0 + Z_{in}} \Rightarrow V_0^+ = \left(\frac{V_0 Z_{in}}{Z_0 + Z_{in}} \right) \frac{1}{e^{jL} + \gamma e^{-jL}}$$

$$V(d) = \left(\frac{V_0 Z_{in}}{Z_0 + Z_{in}} \right) \left(\frac{e^{jd} + \gamma e^{-jd}}{e^{jL} + \gamma e^{-jL}} \right)$$

$$Z_{in} = Z_0 \left(\frac{Z_L + \tanh(jL)}{1 + Z_L \tanh(jL)} \right)$$