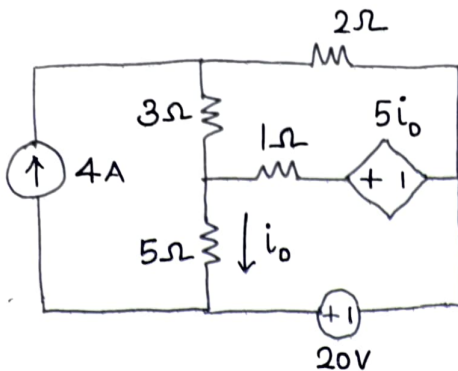


## Problem Set - 2

06 August 2024 10:44


①




a) What kind of a dependent source is there in the circuit?

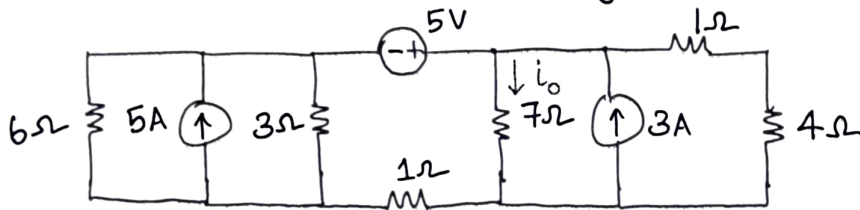b) Find  $i_o$  in the circuit using superposition.

② Find  $i_o$  in the circuit below using source transformation.




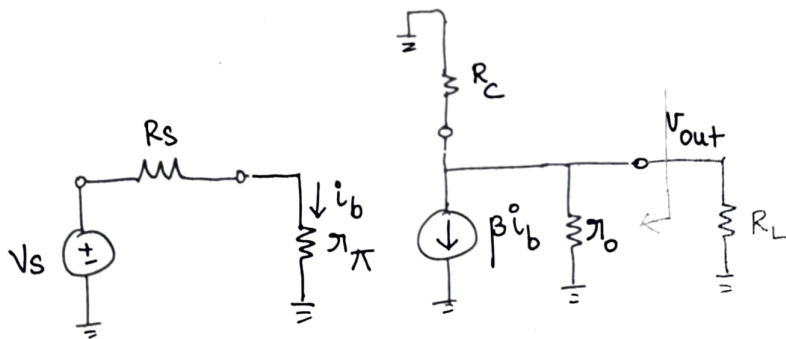
③ Find the Thevenin & Norton equivalent of the following circuit (at  $V_{out}$ ). Do both independently for good practice.




Have you seen the circuit in the box somewhere?

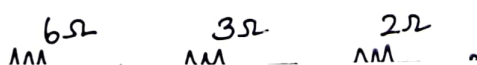④ Find the value of  $R_L$  for maximum power transfer (to  $R_L$ ) in the circuit.



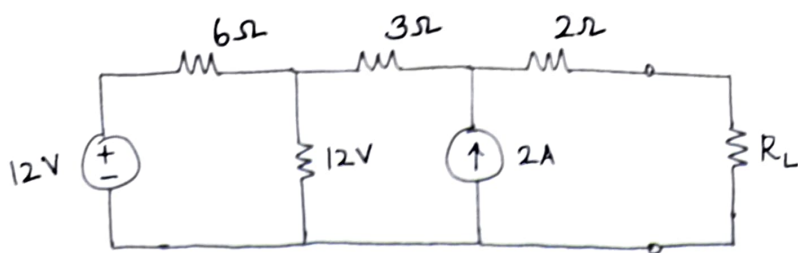


⑤

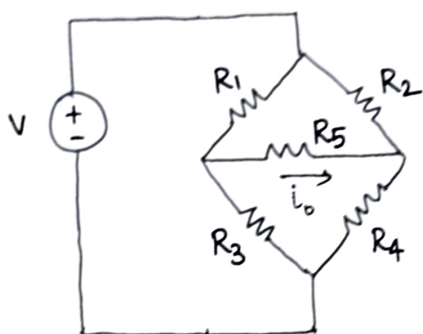


Assume  $R_1$ ,  $R_2$  and  $R_3$  are fixed resistances.

How do you choose  $R_4$  so that  $i_o = 0$ ?

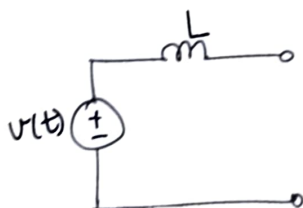⑥ Find the equivalent Norton representation of the following circuits



(a)

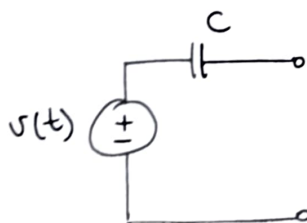

(b)

⑦ Solve the following problems from the book (called as HKD)

"Engineering Circuit Analysis" by Hayt, Kemmerly and Durbin, 8e Indian edition.

(a) Pg: 159 . Problem 1

(b) Pg: 161 . Problem 9

(c) Pg: 169 . Problem 51

(d) Pg: 170 . Problem 56 (We have not covered this in class but it is a useful technique to know).