


ECC-205 NETWORK THEORY

Tutorial - 2


① A constant current of 3A for 4 hours is required to charge an automotive battery. If the terminal voltage is $10 + t/2$ (V) where 't' is in hours

(a) How much charge is transported as a result of the charging?


(b) How much energy is expended?

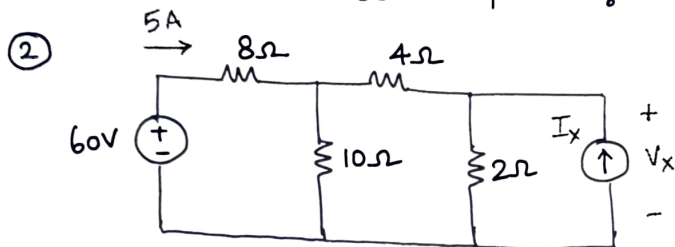


Find V_x and I_x

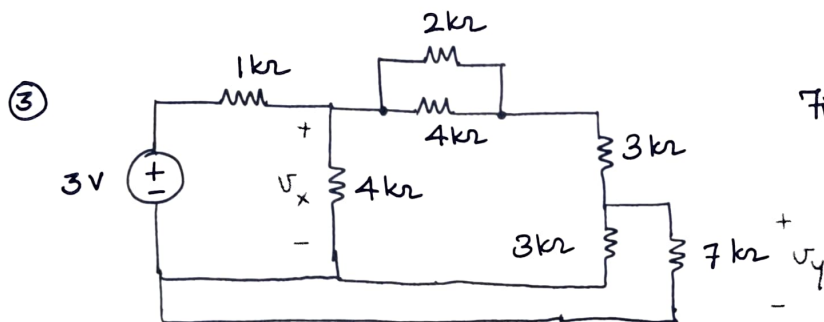

Find V_x and V_y

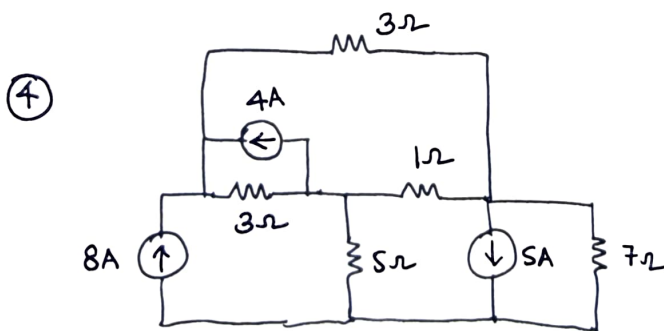

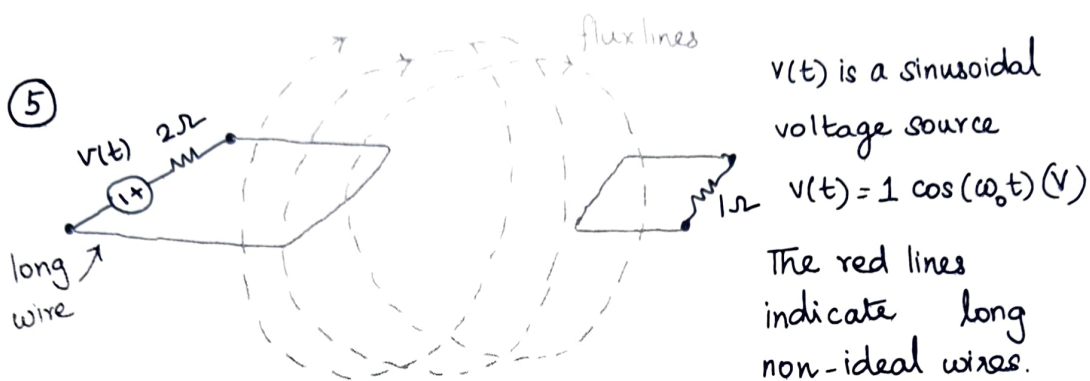Calculate the power absorbed/dissipated by each of the element in the circuit.



If 30% of the magnetic flux lines generated in the circuit on the left, passes through the loop on the right, calculate the power dissipated in the 1Ω resistor.

