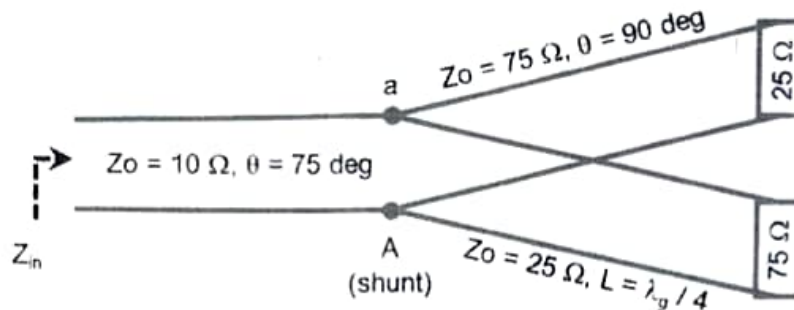


Total Marks: 25

Duration: 1.5 hours


1. Find the input impedance (Z_{in}) and input reflection co-efficient (Γ_{in} with respect to 50Ω reference at input) for the circuit given below (analytically, without using Smith Chart):

5 Marks




2. Find the load impedance (Z_L) for the circuit given below:

5 Marks

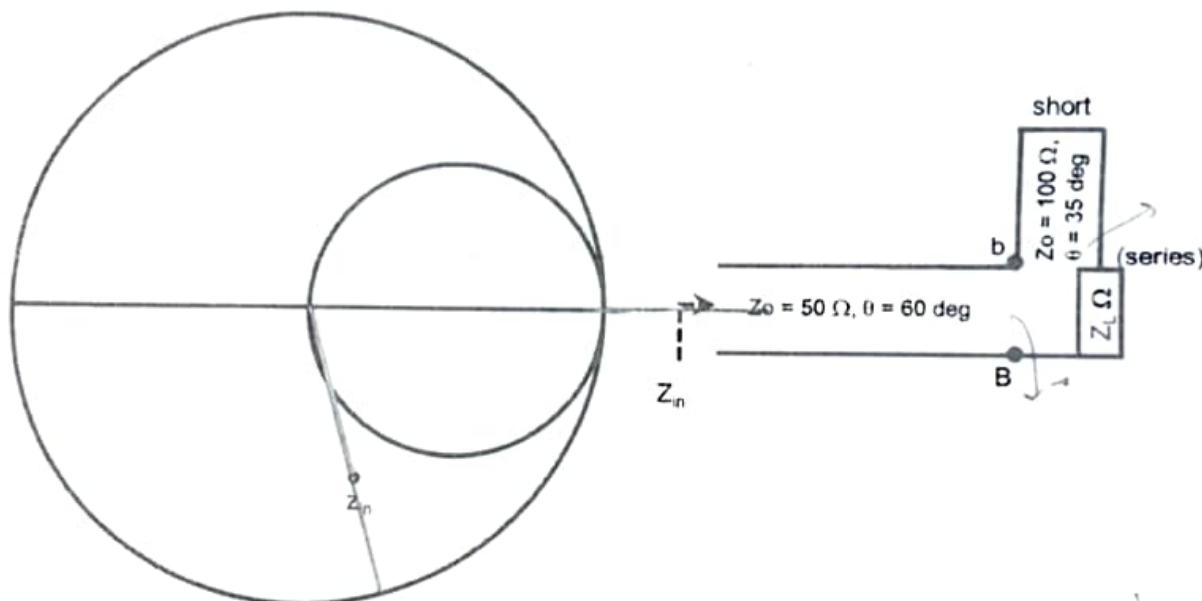


3. Determine the voltage across the load (R_2 , 25Ω) and current through the load in phasor notation for the circuit below:

5 Marks

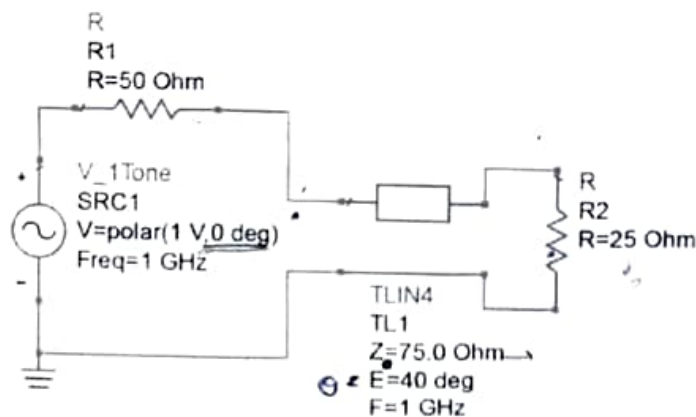


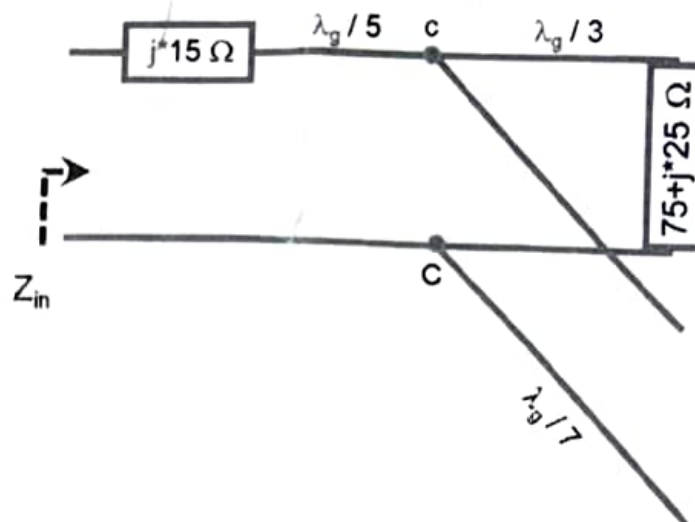4. Find the input impedance (Z_{in}) for the circuit given below using Smith Chart :



$Z_0 = 50$

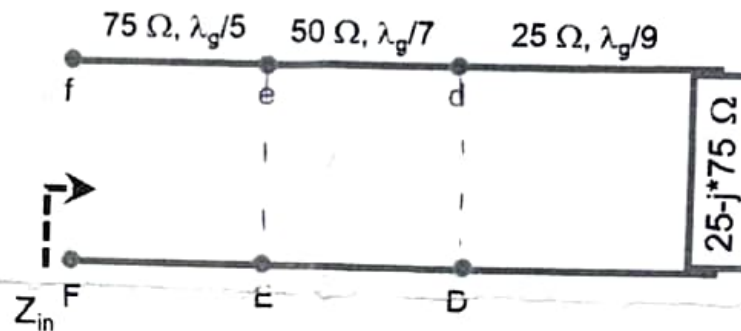5. Find the input impedance (Z_{in}) for the circuit given below using Smith Chart :



Useful formula :

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)}$$